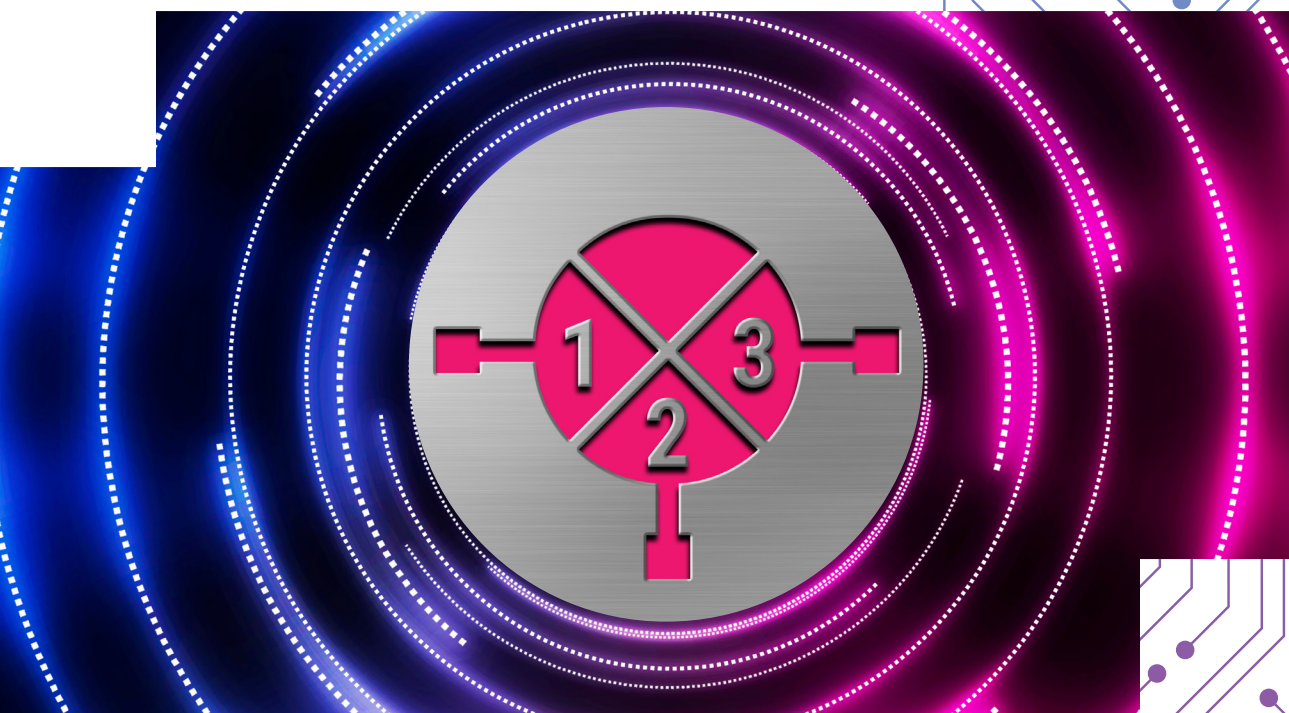




PRIMER

Mixer Basics



By Ferenc Marki & Christopher Marki, Ph.D

Posted Mon May 08 2023

Updated in May 2026

Microwave mixers translate the frequency of electromagnetic signals. This functionality is vital for an enormous number of applications including military radar and surveillance, radio astronomy, and biological sensing. Despite their ubiquity, however, microwave frequency mixers remain one of the most misunderstood components available in the RF/microwave engineer's toolbox. This Mixer Basics Primer intends to shed light on the "dark art" of microwave mixers to help users better understand, select, and ultimately implement Marki Microwave® mixers.

I. WHAT IS A MIXER?

A frequency mixer is a 3-port electronic circuit. Technically, all three ports of a mixer behave as both a load and a source; however, it is generally considered that two of the ports are "input" ports, and the other port is an "output" port.¹ The ideal mixer "mixes" the two input signals such that the output signal frequency is either the sum or difference of the frequency inputs. This concept is shown in **Equation 1**.

$$f_{\text{out}} = f_{\text{in1}} \pm f_{\text{in2}} \quad (1)$$

The nomenclature for the 3 mixer ports is the local oscillator (LO) port, the radio frequency (RF) port, and the intermediate frequency (IF) port. The LO port is typically driven with either a sinusoidal continuous wave (CW) signal or a square wave signal. The choice to apply a CW or square wave signal depends on the application and the mixer. Conceptually, the LO signal acts as the "gate" of the mixer in the sense that the mixer can be considered "ON" when the LO is a large voltage and "OFF" when the LO is a small voltage. The LO port is exclusively used as an input port.

The other two ports of the mixer, the RF and IF, can be interchanged as either the second input or the output; the configuration depends on the application. When the desired output frequency is lower than the second input frequency, the process is called downconversion, where the RF is the input and the IF is the output. The relationship between input and output frequencies is given by **Equation 2**.

$$f_{\text{IF}} = |f_{\text{LO}} - f_{\text{RF}}| \quad (2)$$

On the other hand, when the desired output frequency is higher than the second input frequency, the process is called upconversion, where the IF is the input and the RF is the output. A frequency domain representation of downconversion and upconversion is illustrated in **Figure 1**.

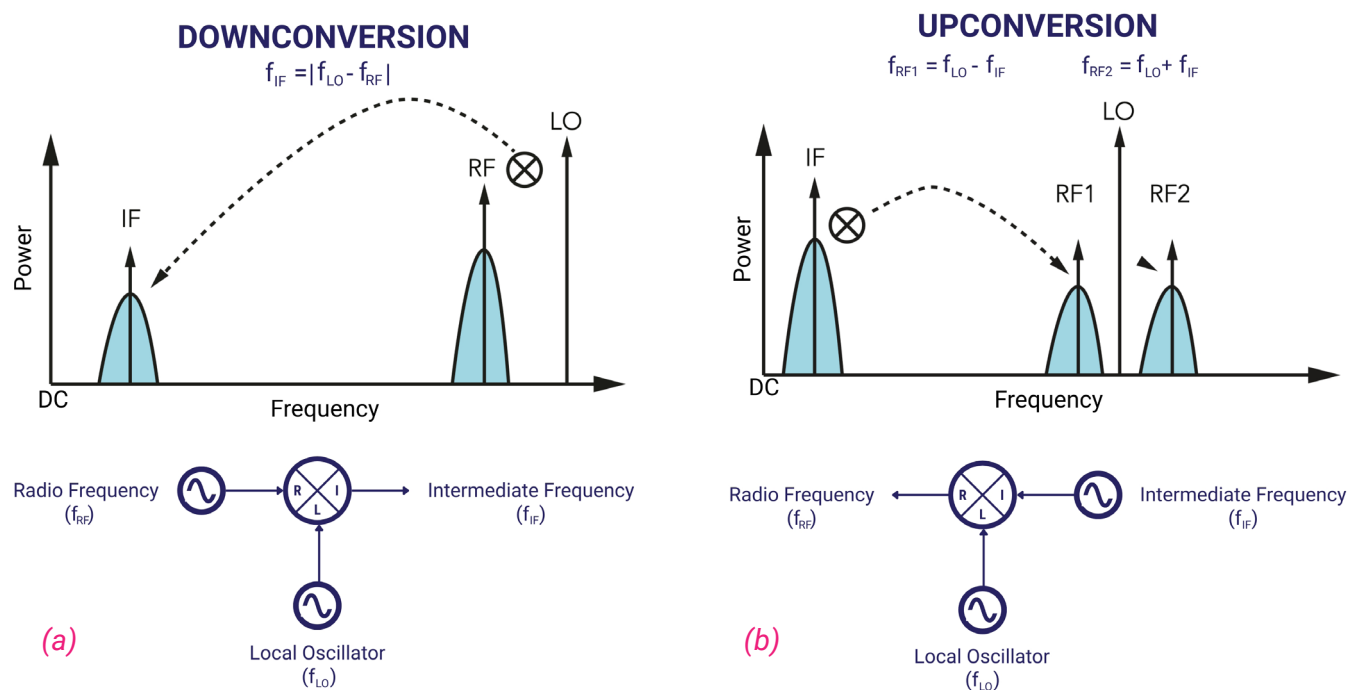


Fig. 1: Definitions of (a) downconversion and (b) upconversion.

Take careful note of the upconversion case; the close proximity of the sum and difference frequencies (f_{RF1} and f_{RF2}) in the frequency domain implies that both are available at the RF output port. This type of upconversion is known as double sided upconversion. Single sided upconversion is also possible, in which case either the sum or the difference frequency is intentionally canceled inside the mixer. Mixers that perform this more sophisticated functionality are called single sideband (SSB) upconverters (or single sideband modulators) and are addressed in “IQ, Image Reject, and Single Sideband Mixer Primer”.² As Figure 1 depicts, IF and RF signals tend to be information bearing signals (as denoted by the broadened spectra surrounding the RF and IF center frequencies). During frequency conversion, the information carried by the RF (IF) signal is frequency translated to the IF (RF) output. Therefore, mixers perform the critical function of translating in the frequency domain.

In principle, any nonlinear device can be used to make a mixer circuit. As it happens, only a few nonlinear devices make “good” mixers. The devices of choice for modern mixer designers are Schottky diodes, GaAs FETs, and CMOS transistors. The choice depends on the application. FET and CMOS mixers are typically used in higher volume applications where cost is the main driver and performance is less important. For the more challenging, high-performance applications, Schottky diode mixers are used almost exclusively. All Marki Microwave mixers are designed using Schottky diode technology. For this reason, this Primer will henceforth focus on diode mixers with only tacit reference to transistor-type mixers.

II. SINGLE DIODE MIXER: IDEAL COMMUTATOR VS. REALISTIC DIODE

There are many ways to build a mixer. The simplest mixer consists of a single diode as shown in **Figure 2a**. A large signal LO and a small signal RF combine at the anode of the diode. For an “ideal” single diode mixer, it is assumed that the LO signal is significantly stronger than the RF signal, such that only the LO signal has the ability to affect the transconductance of the diode. The assumption is that the diode switches instantaneously, as shown in **Figure 2b**. Devices that possess such instantaneous transconductance switching are called ideal commutators and yield the theoretically optimal diode mixer performance.

The “mixing” process takes place due to the switching response of the diode I-V curve to the strong LO signal. As the diode is forced open and closed by the LO, the small signal RF is “chopped”. The analysis of Fourier components of the output signal from a commutating (or switching) mixer diode (**Figure 3a and Figure 3b**) show that the possible output products follow **Equation 3**.

$$f_{IF} = nf_{LO} \pm f_{RF} \text{ (n is ODD only)} \quad (3)$$

Thus, in the ideal case of a perfectly switching commutator, only odd harmonics of the LO are allowed to mix with the fundamental RF tone. Unfortunately, the transfer function of the ideal commutator can never be achieved in the real world. Actual Schottky diodes necessarily possess some amount of “turn-on” transition, as shown in **Figure 2c**.

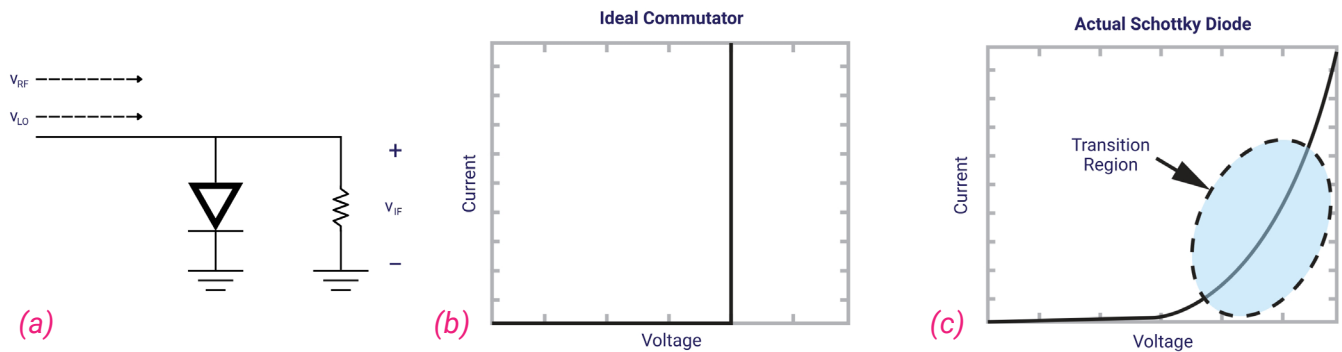


Fig. 2: (a) Simple single ended mixer. I-V characteristics for (b) the ideal commutator and (c) a realistic Schottky diode.

In addition to the diodes requiring an amount of “turn-on” transition, the RF signal will modulate the diode transconductance to some extent, even if the RF is very small. The combination of realistic diode I-V characteristics and transconductance modulation by the RF signal causes additional mixing products (often referred to as “spurs”). Hence, realistic diodes produce all possible harmonic mixing components. The time domain signal and associated frequency spectrum generated by a realistic Schottky diode are depicted in **Figure 3c and Figure 3d**. Mathematically, the frequency components generated by a single diode are given by **Equation 4**.

$$f_{IF} = nf_{LO} \pm mf_{RF} \text{ (m and n are ALL integers)} \quad (4)$$

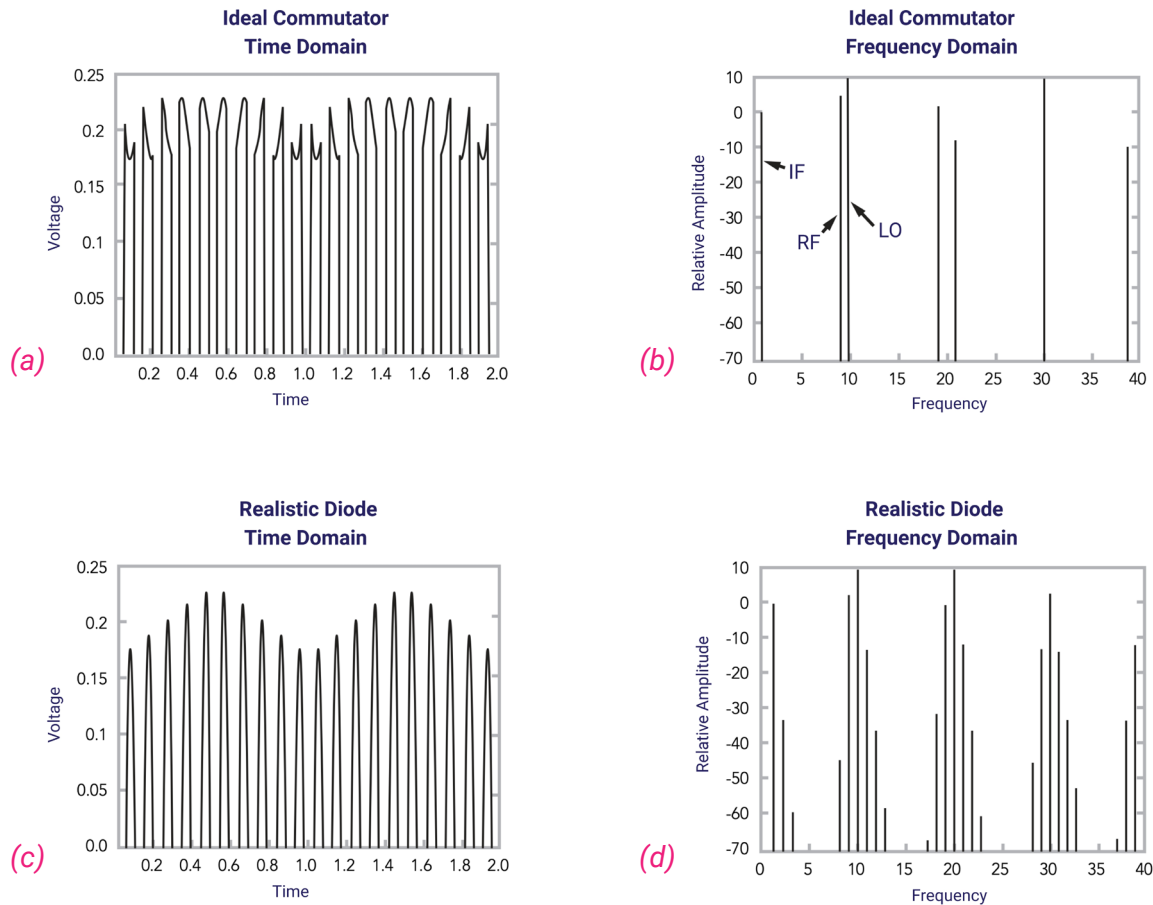


Fig. 3: The output of an (a) ideal commutator in time domain, (b) ideal commutator in the frequency domain, (c) realistic diode in the time domain, and (d) realistic diode in the frequency domain.

Because users only want one desired output frequency (when $n=1$ and $m=1$), the existence of all other harmonic terms creates significant problems. Elimination of these distortion products is a key goal in mixer design.

This simplified analysis illustrates several important trends in frequency mixers:

1. “Mixing” is caused by the switching behavior of the diode.
2. The majority of unwanted harmonics are caused by the nonlinear intermodulation of the RF and LO signals in the transition region of the diode.
3. An “optimal” diode mixer will possess diodes that closely approximate the ideal commutator.
4. The lower the RF power, the better the spurious performance (since the LO will control the diode transconductance more effectively).

III. MIXER BALANCE

High performance mixers are designed using four and sometimes eight diodes. The evolution of the mixer circuit from the single diode unbalanced type to the multi-diode balanced type is described here.

Sophisticated mixer designs make use of circuit symmetry to create “balance”. In fact, nearly all commercially available mixers make use of some kind of mixer balancing. Mixer balancing offers several advantages, including inherent isolation between all mixer ports (and hence band flexibility), cancellation of most intermodulation products, common mode signal rejection, and improved conversion efficiency.

In mixers, extra circuitry is needed to route and separate (i.e. multiplex) input and output signals from the diodes; such is the cost for using a two terminal device to perform a three-port functionality. In single diode mixers, this extra circuitry typically comes in the form of some kind of passive coupling, power division, and/or filtering. It is difficult to create wideband single diode mixers with independent RF, LO, and IF bands since the multiplexing circuitry is frequency specific. Moreover, such circuitry causes extra losses that reduce mixer efficiency.

To solve this problem, engineers realized that wideband single-balanced mixers with low loss and independent input and output frequency bands could be created using the classic four port hybrid junction. The hybrid junction (a.k.a. the “magic tee” or the 180° hybrid), depicted in **Figure 4a**, is a two input, two output, four port circuit that provides mutual isolation between input ports and equal power division at the output ports. The applicability of the hybrid junction for mixers is apparent: the input LO and RF sources will be isolated from one another, thus providing frequency band independence and equal power division to the load. The input/output transfer characteristics are listed in **Figure 4b**. Notice that the output signals are differentially phased (i.e. 180° phase shifted) when a signal is input to port 2. Output signals are in phase for inputs into port 1.

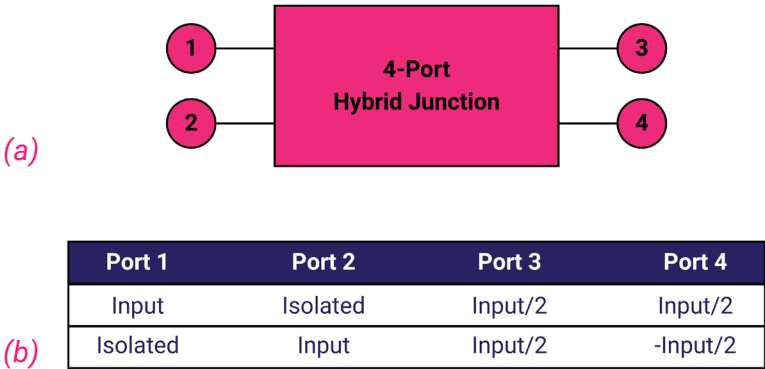


Fig. 4: a) Schematic and b) I/O table for a 4-port hybrid junction.

The hybrid junction provides a natural method by which to create the single balanced mixer, as shown in **Figure 5**. Additionally, two diodes are used instead of one. Key features of the single balanced mixer include:

1. Isolation (and hence frequency independence) between RF and LO ports.
2. 50% reduction in the total number of intermodulation products.
3. Common mode noise cancellation (good for noisy LOs).
4. Higher conversion efficiency than the single diode mixer.



Fig. 5: Single balanced mixer with 4-port hybrid junction.

Further, two single balanced mixers combine to form the double balanced mixer, as shown in **Figure 6**. In this case, hybrid junctions are placed on both the RF and LO differential ports, and the IF signal is obtained at the in-phase port of the hybrid junction. The reciprocity of the hybrid junction allows this type of interconnection. Detailed analysis reveals that for the double balanced mixer, only ODD n and ODD m harmonic spurs can survive at the IF port.¹ Therefore, mixer double-balancing has the benefit of reducing nearly 75% of the spurious interferers possible at the IF port. Due to the conservation of energy, double balanced mixers tend to have better conversion efficiency than single ended or single balanced mixers since energy cannot spread into the EVEN order harmonics.

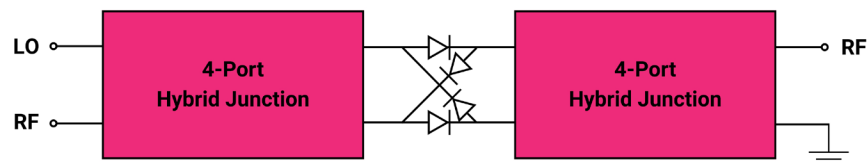


Fig. 6: Double balanced mixer.

A more complex mixer circuit is created using two double balanced mixers driven in a push-pull configuration (**Figure 7**). This “doubly double balanced” mixer has received the ill-conceived title of the “triple balanced” mixer. Some of the key features of the triple balanced mixer are overlapping RF, LO, and IF bands and higher spurious suppression. Marki Microwave T3 mixers are a special subset of triple balanced mixers and provide the highest spurious suppression possible by closely emulating the ideal commutator switching behavior.

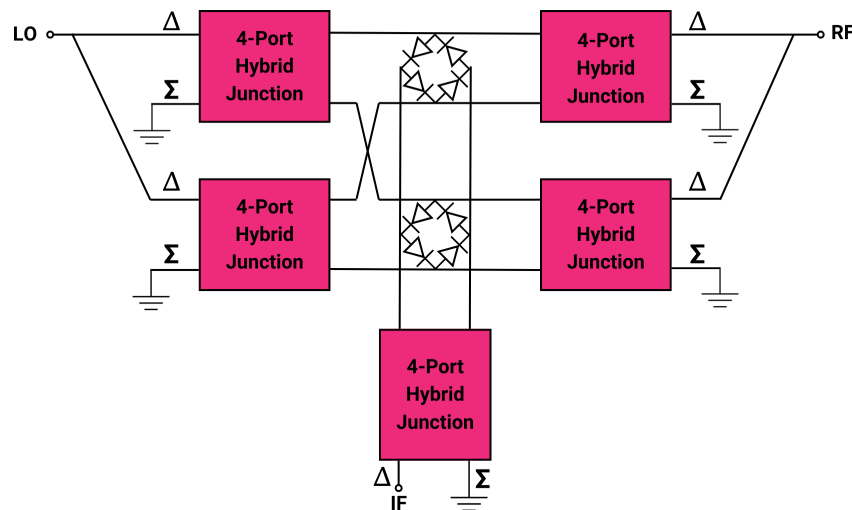


Fig. 7: Schematic of a doubly double balanced mixer (i.e. triple balanced mixer).

IV. MIXER PERFORMANCE METRICS

Many attributes contribute to a “good” mixer design. This section addresses some of the criteria by which to judge, and ultimately choose, a mixer.

A. Conversion Loss

The most important mixer metric is conversion loss (CL). Conversion loss is defined as the difference in power between the input RF power level and the desired output IF frequency power level, as shown in **Equation 5**.

$$CL = P_{RF} - P_{IF} \quad (5)$$

where P_{RF} and P_{IF} are in dBm and CL is in dB. For example, if the input RF is -10 dBm and the downconverted IF output signal -17 dBm, then the conversion loss is 7 dB.

The theoretically optimum conversion loss for a passive diode mixer is 3.9 dB and can be calculated using equations derived by Henderson.³ Typical values of conversion loss range between about 4.5 to 9 dB, depending on the mixer. The additional losses are caused by factors such as transmission line losses, balun mismatch, diode series resistance, and mixer (im)balance. In general, double balanced mixers outperform triple balanced mixers in terms of conversion loss due to smaller circuit losses. Another important trend is that wider bandwidth mixers tend to have higher conversion loss due to the difficulty in maintaining circuit balance over the entire bandwidth.

Conversion loss is the benchmark mixer metric because it correlates closely with other metrics like isolation and 1 dB compression. Experience shows that for a mature mixer design such as the Marki Microwave MM1-0222, a single conversion loss measurement can suffice in diagnosing the quality of the unit. Hence, as long as the conversion loss of the unit remains tightly within spec, other measurements are not as critical since experience shows that all other metrics will also fall within spec. The converse is not necessarily true however; for example, it is possible to have good isolation

and poor conversion loss. Therefore, conversion loss is the benchmark measurement for all mixers. Marki Microwave tests the conversion loss of all mixers produced in the facility.

B. Isolation

Isolation is a measure of the amount of power that leaks from one mixer port to another. As was described previously, port isolation is obtained through mixer balance and the use of hybrid junctions. Unfortunately, there will always be some small amount of power leakage between the RF, LO, and IF ports. Isolation is the difference in power between the input signal and the leaked power to the other ports. In other words, if we place an input signal at the LO port and measure the power available at the RF port at that LO frequency, the isolation in dB is given by **Equation 6**.

$$P_{\text{ISO (L-R)}} = P_{\text{in(@LO)}} - P_{\text{out(@RF)}} \quad (6)$$

Note that isolation is approximately reciprocal: the port 1 to port 2 isolation will track closely with the port 2 to port 1 isolation. Hence, a single measurement can be performed to determine the isolation in both directions.

Three types of isolation are commonly quoted in microwave mixers: L-R isolation, L-I isolation, and R-I isolation. The definitions of each type of isolation are illustrated in **Figure 8**.

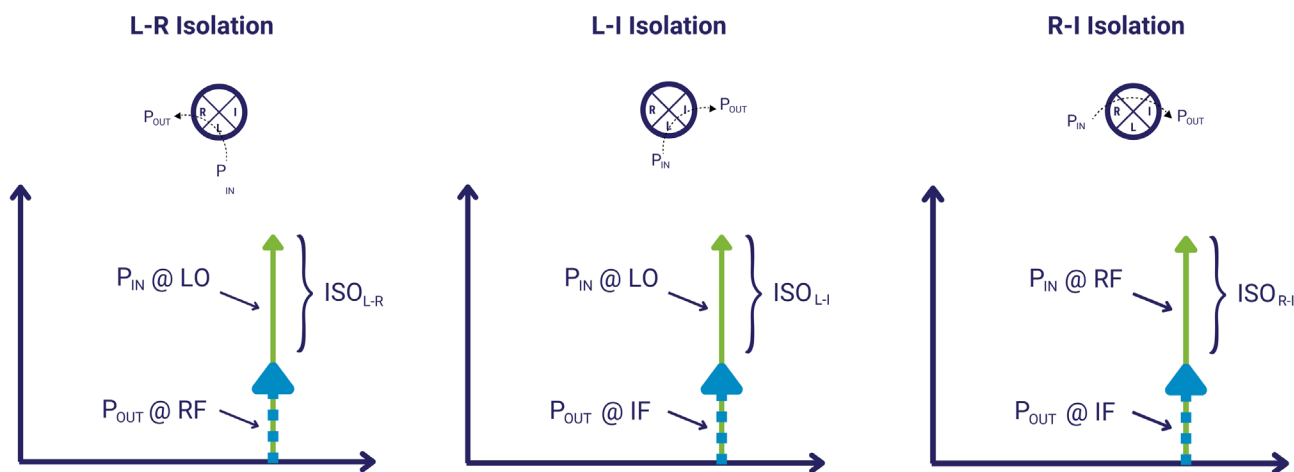


Fig. 8: Definitions of mixer isolation for L-R, L-I, and R-I isolation.

L-R isolation is the leakage of the LO into the RF port. Typical L-R isolation values range between about 25 to 35 dB. L-R isolation is critical in frequency downconversions because LO power can leak into the RF circuitry. If L-R isolation is poor, LO power can contaminate the RF line by either interfering with the RF amplifier or by leaking to other parallel mixing channels causing cross-channel interference. Poor L-R isolation can also cause problems in frequency upconversions when the LO frequency is very close to the RF output frequency (i.e. the IF frequency is at or near DC). In this case, no amount of filtering can separate the arbitrarily close RF signal and LO leakage. This can result in interference between the RF and LO and a degradation in the RF output circuitry.

L-I isolation is the leakage of the LO into the IF port. L-I isolation tends to be the worst of the three types of mixer isolation, with typical values ranging from 20 to 30 dB. The most critical consequence of poor L-I isolation arises when the LO and IF frequencies are close together, as the LO can directly contaminate the IF circuitry. Another significant problem occurs when the LO leakage is strong enough to saturate the IF amplifier. Additionally, poor L-I isolation is known to cause conversion loss flatness problems.

The final mixer isolation metric is R-I isolation. Values of R-I isolation typically range from 25 to 35 dB. Most systems designers will not find R-I isolation to be a major issue since the RF and IF powers tend to be orders of magnitude smaller than the LO power. Therefore, LO isolation problems are the primary concern of systems engineers. R-I isolation, instead, is a major concern for mixer designers because it serves as a diagnostic metric for the overall conversion efficiency of the mixer circuit. When the R-I isolation is high, the mixer circuit is well balanced, and thus the conversion loss tends to be low. In mixers with bad R-I isolation (<20 dB), the conversion loss is higher, and the conversion loss flatness is poor.

C. 1 dB Compression

Under normal (linear) operation, the conversion loss of the mixer will be constant, regardless of input RF power. If the input RF power increases by 1 dB, then the output IF power will also increase by 1 dB (and the power difference is the conversion loss). However, as the RF power becomes too large, this dB for dB relationship will not hold. The 1 dB compression point is a measure of the linearity of the mixer and is defined as the input RF power required to increase the conversion loss by an extra 1 dB from ideal.

Mixer compression is most easily represented graphically, as shown in **Figure 9**. For low input RF power, the slope of the line is 1:1, as described above. However, as the RF power increases, the mixer deviates from this linear behavior, and the conversion loss starts to increase. When the input/output curve “sags” by 1 dB (i.e the conversion loss increases by 1 dB), the input RF 1 dB compression has been reached.

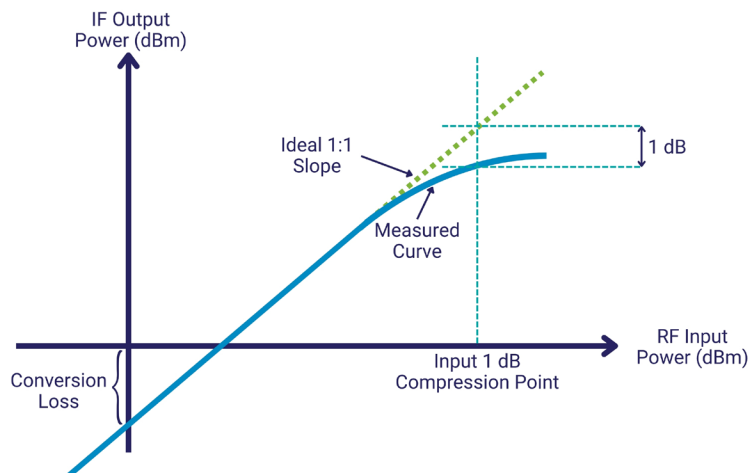


Fig. 9: Graphical representation of 1 dB compression point.

Conceptually, the 1 dB compression point occurs when the RF signal can no longer be considered “small signal”. Under linear operation, the LO power is so much stronger than the RF power that the diode switching action is totally dominated by the LO, as described in Section 2. However, in compression, the RF power is commensurate with the LO power such that the diode switching action is compromised. When the RF power is too high, the mixer balance degrades and the mixer circuit behaves like a single diode mixer. Among other things, operating the mixer in compression causes increased levels of intermodulation distortion, higher conversion loss, and degraded isolation performance. This behavior occurs because the compressed mixer spreads energy in the frequency domain, due to the diodes being partially turned-on by the RF signal. Slight mixer imbalances are therefore exacerbated, and the mixer conversion efficiency is degraded.

Mixer compression can be improved by using higher turn-on diodes. In this way, a larger RF power can be applied to the mixer without challenging the turn-on voltage of the diode. The trade-off, of course, is that a larger LO drive must also be applied to switch the diode ON and OFF. As a general rule of thumb, the 1 dB compression point will be anywhere from 4 to 7 dB below the minimum recommended LO drive level of the mixer. For low barrier “L” diodes, 1 dB compression occurs for input RF powers > 0 dBm. For super-high barrier “S” diodes, 1 dB compression occurs for input RF power $> +12$ dBm. State-of-the-art mixers such as the T3 series can be driven with any LO power > 15 dBm and the corresponding 1 dB compression point will be 3 to 4 dB below that drive. For example, a T3 driven with $+18$ dBm will compress around $+15$ dBm. That same T3 driven with $+25$ dBm will compress around $+22$ dBm. To Marki Microwave’s knowledge, no other mixer created offers the ability to linearly increase the 1 dB compression point simply by increasing the LO drive level.

D. VSWR

Mixer VSWR is a contentious topic. It is a Marki Microwave opinion that VSWR is a meaningless metric for microwave mixers because it does not help to predict mixer performance, nor does it guarantee proper operation when the mixer is integrated within the surrounding RF system. The crux of the argument comes down to the fact that the mixer cannot be modeled as a static load. In actuality, a mixer is both a load and a source. In fact, it can be easily shown that all three mixer ports act as sources for the intermodulation distortion intrinsic to the diodes.¹ Even if the VSWR of the mixer is perfect (i.e. no reflections of the fundamental), there will inevitably be harmonics coming out of the input ports.

A classic mixer spur problem involves the $2 \times \text{LO} \times 1 \times \text{RF}$ “image” spur. It can be shown that all EVEN LO $\times$ ODD RF spurs generated within the mixer are available at the RF port.¹ A problem arises when the RF port is reactively terminated with, for example, a preselection bandpass filter. Acting as a source, the mixer produces the $2L \times 1R$ image spur which exits the RF port and enters the RF filter. Most commonly, the $2L \times 1R$ product will lie outside the passband of the filter and will hence be reflected back into the mixer as shown in **Figure 10**. Upon re-entry into the mixer, the $2L \times 1R$ image product will mix with the LO and downconvert to the exact same frequency as the desired difference frequency, as shown mathematically in **Equation 7**.

$$\begin{aligned}
 f_{\text{out}} &= f_{\text{spur}} - f_{\text{LO}} \\
 f_{\text{out}} &= 2f_{\text{LO}} - f_{\text{RF}} - f_{\text{LO}} \\
 f_{\text{out}} &= f_{\text{LO}} - f_{\text{RF}} \\
 f_{\text{out}} &= f_{\text{IF}}
 \end{aligned}
 \tag{7}$$

The overlap of the downconverted image spur and the desired IF creates substantial interference. The extent of the interference depends on the relative phase difference between the two signals. If the RF frequency is swept, the relative phase will cycle from 0 to 2π , resulting in significant conversion loss ripple. A common concern is that poor mixer VSWR causes conversion loss ripple. However, as illustrated in this example, issues associated with the mixer acting as a source of RF and LO products frequently lead to more serious problems if precautions are not taken.

All Marki Microwave mixer specifications are defined assuming wideband 50 Ω systems. In Marki's experience, mixer VSWR is a minor concern compared to the myriad of problems that arise when the mixer ports are reactively terminated, such as in the above example. To solve these problems, Marki recommends increasing attenuation or using non-reflective terminations such as absorptive low pass filters or 50 Ω terminated diplexers.

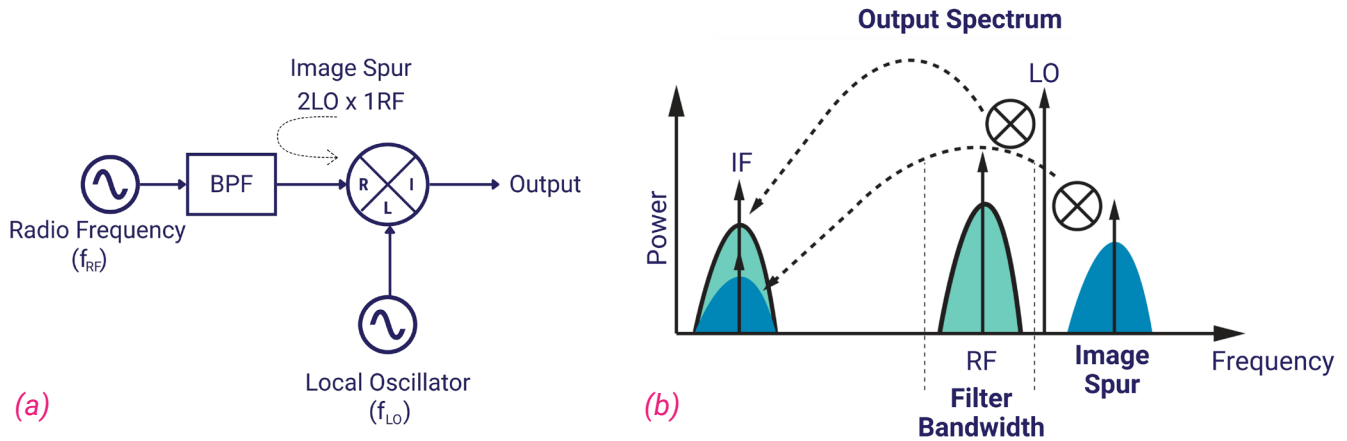


Fig. 10: (a) Schematic diagram showing backreflected $2f_{\text{LO}} \times f_{\text{RF}}$ spur from reactive bandpass filter (BPF) and (b) output spectrum showing desired IF and downconverted image spur overlapping in frequency.

E. Noise Figure

As long as the quality of the diode is closely monitored, the noise figure of the mixer can be approximated by the conversion loss. Generally, the cumulative noise figure will limit the minimum detectable signal in the receiver. Hence, when choosing mixers for low power applications, conversion loss should be as low as possible.

F. Single-tone Intermodulation Distortion

Equation 3 and Figure 3 previously demonstrated the harmonic mixing products generated by the nonlinear mixing of the RF and LO signal in the transition region of the diode I-V curve. Most commonly, the only desirable mixing term is given by $m=1$ and $n=1$ in Equation 3, and all other unwanted harmonic terms are called single-tone IMD. A major goal in mixer design is to limit the strength of the single-tone IMD terms.

The key features of single-tone IMD in double and triple balanced mixers are:

1. Only ODD n by m terms exist at the IF port in double and triple balanced mixers.
2. Cancellation through mixer balance improves EVEN by EVEN, EVEN by ODD, and ODD by EVEN harmonic levels by approximately 30 dB.
3. The lower the RF input power, the better the single-tone spurious performance.
4. With the exception of the T3 mixer, increasing the LO drive does not always improve spurious performance.

Marki Microwave provides typical mixer spur tables for its double balanced, triple balanced, and T3 mixer lines. For additional information on single-tone IMD in double balanced mixers, see Henderson's analysis on the prediction of mixer IMD.³

G. Multi-tone Intermodulation Distortion

Multi-tone intermodulation distortion (IMD) implies that multiple tones enter the mixer through the same port and intermodulate in the mixer diodes. Multi-tone IMD is a form of common mode mixing in which two or more tones enter the RF port and nonlinearly mix with each other and the LO to create distortion, as shown in **Figure 11**. From the perspective of a system designer, multi-tone IMD is a serious problem because it can generate interference tones that fall within the IF bandwidth of the receiver. Hence, multi-tone IMD places a theoretical upper limit on the dynamic range of the receiver.

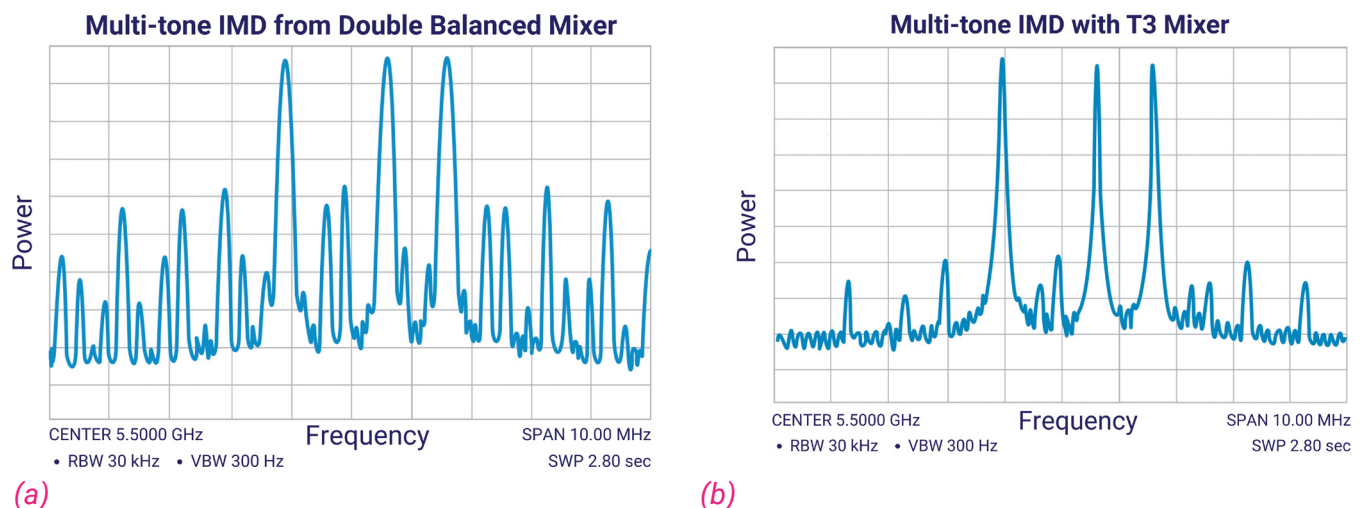


Fig. 11: (a) Significant multi-tone IMD caused by three input RF signals.
(b) Improved IMD performance using a T3 mixer due to commutating diode behavior.

The efficiency of multi-tone IMD generation is dependent on the intrinsic nonlinear characteristics of the devices (i.e. diodes, FETs, etc.) and the balance of the mixer. The widely accepted figure of merit for mixer multi-tone performance is the two tone third order input intercept point (TOI). Also referred to as “two-tone” IMD and by the acronym IIP3, TOI is a mathematical construct used in predicting the nonlinear behavior of a mixer as the input RF power increases. The generation of two-tone products is illustrated in **Figure 12**. Two closely spaced signals enter the RF port of the mixer and nonlinearly intermodulate with the LO. The possible harmonics available at the mixer IF port are given by **Equation 8**.

$$f_{out} = \pm n f_{LO} \pm m_1 f_{RF1} \pm m_2 f_{RF2} \quad (8)$$

where n , m_1 , and m_2 are all integers. As is shown in Figure 11, two-tone IMD is troublesome because the generated interference tones overlap in frequency with the desired downconverted signals. No amount of filtering can separate the two-tone interference, and thus the signal to noise ratio of the received signal is degraded.

While fundamental mixing tones (i.e. $m=1$ and $n=1$) grow by a slope of 1 to 1 with input RF power, higher order RF mixing terms grow by a slope of $m:1$. In the case of Equation 7, two-tone IMD grows by a slope of $|m_1| + |m_2|$ to 1. Hence, interference terms in **Equations 9a and 9b** are called third-order IMD products and grow by a slope of 3:1, as shown in **Figure 13**.

$$\text{Interferer}_1 = 2f_{RF1} - f_{RF2} - f_{LO} \quad (9a)$$

$$\text{Interferer}_2 = 2f_{RF2} - f_{RF1} - f_{LO} \quad (9b)$$

Graphically, the input power at which the fundamental (1:1) line and the interference (3:1) line intersect is the third order intercept (TOI) point. It is notable that the TOI is an extrapolated point because the mixer would compress before the lines crossed. Nevertheless, the impact of the third-order interference products can be debilitating in many systems at RF power well below the 1 dB compression point. The higher the TOI, the better the mixer.

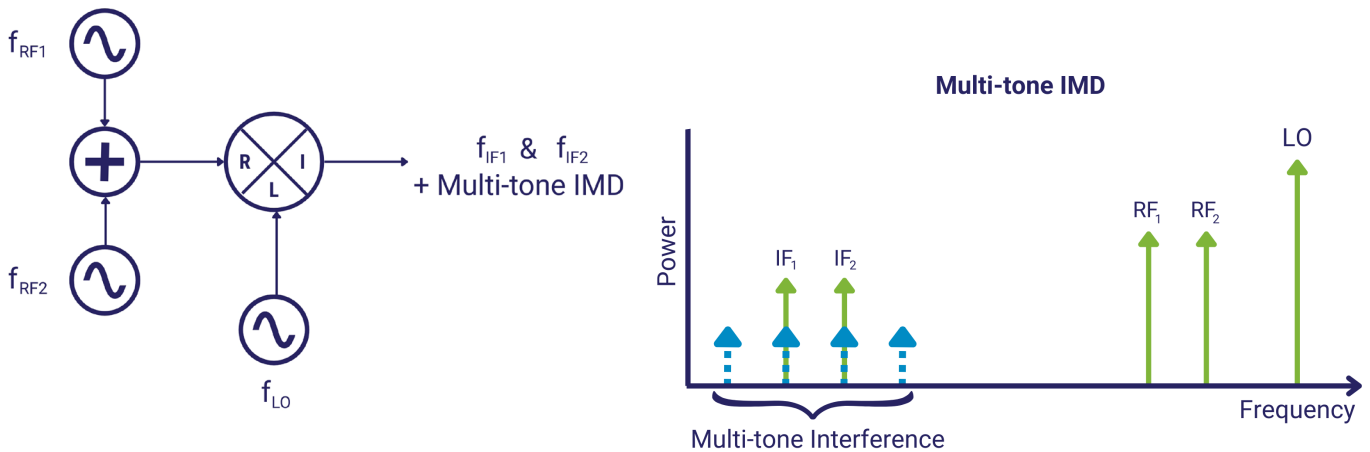


Fig. 12: Illustration of multi-tone IMD created by two closely spaced RF signals. Generated IMD tones overlap with desired IF_1 and IF_2 signals.

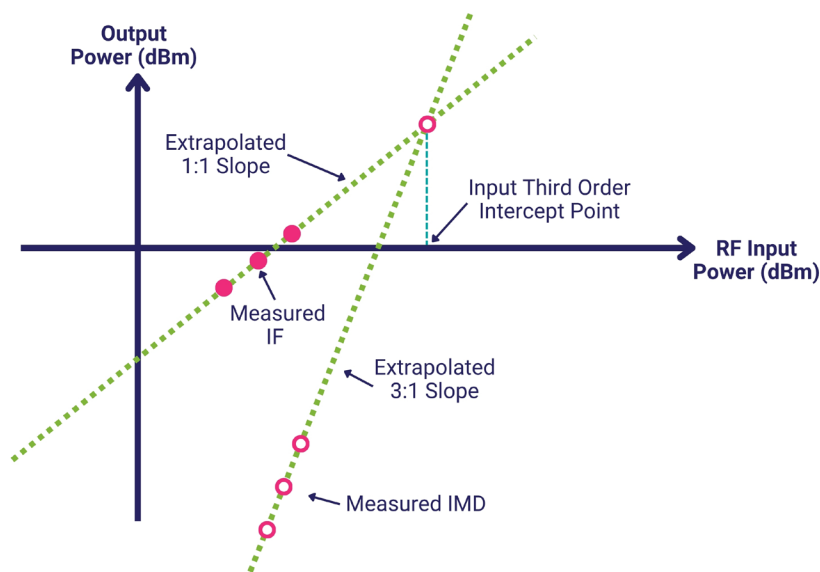


Fig. 13: Third order IMD products.

Typical values of TOI can vary dramatically depending on the mixer type and technology. Conventional double balanced and triple balanced mixers tend to have TOI values a few dB above the recommended drive level. For example, a Marki Microwave M2-0220 triple balanced mixer with medium barrier (“M”) diodes requires at least +13 dBm of LO drive. The corresponding TOI at this drive level is +18 dBm. For state-of-the-art TOI performance, Marki Microwave recommends using the T3 mixer. The T3 mixer provides unprecedented bandwidth and IMD performance compared to all other mixer lines (offered by Marki or elsewhere) because the diodes are designed to behave much more closely to the ideal commutator described in Section 2. The argument is simple: if the RF tones are not capable of switching the diode from the OFF to the ON state, as is the case in the ideal commutator, then no multi-tone interference is possible. This fact is vividly demonstrated in Figure 11. Figure 11a was measured using a standard double balanced M1 mixer. Figure 11b was measured using a T3 mixer. The commutating diode concept is so powerful that T3 mixers can easily achieve TOI greater than +30 dBm for LO drives below +20 dBm.

V. SUMMARY

The sole purpose of the microwave mixer is to provide either the sum or difference frequency of the two incoming signals at the output. The goal of a mixer designer is to create a circuit that performs this frequency translation efficiently and without distortion. For optimal performance, hybrid mixers using Schottky diodes remain the technology of choice for state-of-the-art system designers. This is due, in part, to the fact that RF/microwave mixer performance is dependent on both the quality of the diodes used and the sophistication of the surrounding circuitry involved. The three-dimensional microwave hybrid assembly approach employed by Marki Microwave is impossible to replace with restrictive two-dimensional integrated circuit fabrication techniques. For this reason, Marki Microwave

draws on over five decades of industry experience to boast the widest selection of high-performance RF/microwave mixers in the world. Between Marki Microwave's double balanced, triple balanced, and T3 mixer families, there is a perfect mixer choice for any application.

VI. REFERENCES

[1] Marki, F.A., "Miniature Image Reject Mixers And Their Use In Low-noise Front-ends In Conjunction With Gaas Fet Amplifiers," Circuits, Systems and Computers, 1977. Conference Record. 1977 11th Asilomar Conference on, pp. 159-162, 7-9 Nov 1977. <http://www.markimicrowave.com/menus/appnotes/noise.pdf>.

[2] Jorgesen, D., "IQ, IR & SSB Mixer Primer," Marki Microwave, Morgan Hill, CA, https://markimicrowave.com/assets/598ea3c3-07ad-4c0c-972f-10e7b4262033/IQ_IR_SSB_Mixer_Primer.pdf, May 13, 2020.

[3] Henderson, B. C., "Predicting Intermodulation Suppression in Double-Balanced Mixers," Watkins-Johnson Company Technical Notes. Vol. 10, No. 4, July/August 1983.

Additional Reading:

Marki, F. and Marki, C., "T3 Mixer Primer: A mixer for the 21st Century", Marki Microwave, Morgan Hill, CA, http://www.markimicrowave.com/menus/appnotes/t3_primer.pdf, 2010.

© 2026. Marki Microwave, LLC. All Rights Reserved. MARKI MICROWAVE, M wave logo, FastSwitch, and T3 MIXER are trademarks or registered trademarks of Marki Microwave, LLC. All other trademarks used are the property of their respective owners.

MARKI MICROWAVE, LLC, ("MARKI") PROVIDES TECHNICAL SPECIFICATIONS AND DATA, APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, AND OTHER INFORMATION AND RESOURCES "AS IS" AND WITH ALL FAULTS. MARKI DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT.

These resources are intended for developers skilled in the art designing with Marki products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards and other requirements. Marki makes no guarantee regarding the suitability of its products for any particular purpose, nor does Marki assume any liability whatsoever arising out of your use or application of any Marki product. Marki reserves the right to make changes to its product(s) or information described herein without notice.